



Printed Pages : 7

TEC-101

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 3033**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech.**

**(SEM. I) EXAMINATION, 2007-08**

**ELECTRONICS ENGINEERING**

*Time : 3 Hours]*

*[Total Marks : 100*

*Note : Attempt all questions.*

- 1 Attempt any four parts of the following : **5×4=20**
- (a) What is the difference between an intrinsic and an extrinsic semiconductor ? Define a hole in a semiconductor.
- (b) Define :
- (1) Donor and acceptor impurities
  - (2) Mobility and conductivity.
- (c) Estimate the relative concentration of germanium atoms and electron hole pairs at 300 K (room temperature). Also predict the intrinsic resistivity. Given atomic weight of germanium, 72.60 g/g-atom,  $e=1.6 \times 10^{-19}$  coulombs intrinsic concentration (at 300 K)  $2.4 \times 10^{19}$  electron-hole pairs/ $m^3$ . Density for germanium =  $5.32 \times 10^6$  g/ $m^3$ . Electron mobility = 0.39, hole mobility = 0.19.





- (d) Determine the number of atoms of aluminium (Al) in cubic meter. Then find the average drift velocity in an Al conductor with a cross-sectional area of  $1 \text{ cm}^2$  carrying a current of  $1 \text{ A}$ .

Given : Atomic weight of Al =  $26.98 \text{ g/g-atom}$ , density of Al =  $2.7 \times 10^6 \text{ g/m}^3$ .

- (e) Explain (i) How does the reverse saturation current of a p-n diode vary with temperature ? (ii) How does the diode voltage (at constant current) vary with temperature ?
- (f) Sketch the piece wise linear characteristics of a diode. What are the approximate cut in voltages for silicon and germanium ?

$V_F \approx 0.7 \text{ V}$   
 $V_G \approx 0.3 \text{ V}$

2 Attempt any two parts of the following :

- (a) Sketch the circuit for a full-wave rectifier using two diodes only. Derive the expression for (i) the dc current, (ii) the dc load voltage, (iii) the dc diode voltage, (iv) the rms current.

- (b) A full wave rectifier with a centre-tapped transformer supplies a dc current of  $100 \text{ mA}$  to a load resistance of  $R = 20 \Omega$ . The secondary resistance of transformer is  $1 \Omega$ . Each diode has a forward resistance of  $0.5 \Omega$ . Determine following :

- (1) rms value of the signal voltage across each half of the secondary
- (2) dc power supplied to the load
- (3) PIV rating for each diode
- (4) ac power input to the rectifier
- (5) conversion efficiency.

- (c) Explain clipping and clamping circuits in detail. For the Zener regulator circuits of Fig. 1 determine the range of input voltage ( $V_s$ ) for the zener diode to remain in "ON" state. Given : Zener diode;  $V_z = 20 \text{ V}$ ,  $I_z(\text{max}) = 50 \text{ mA}$ ,  $R_z = 0$ .

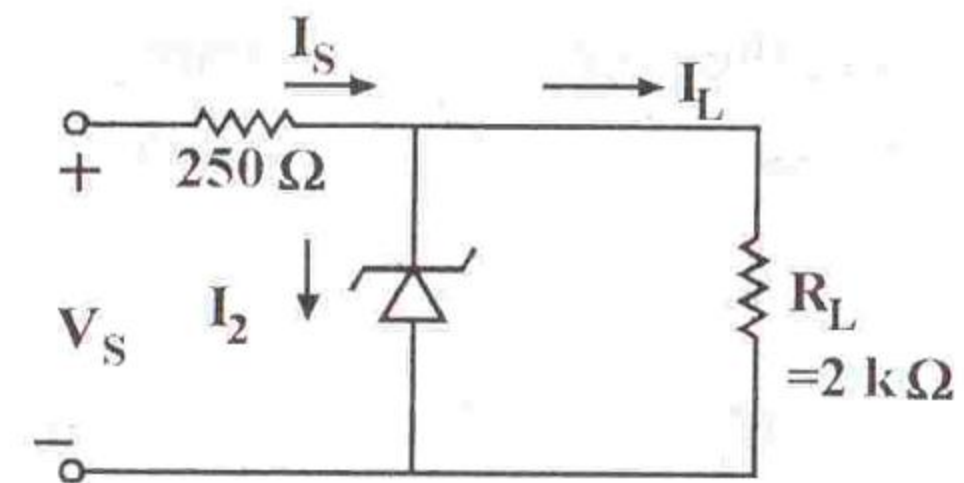


Fig. 1

3 Attempt any two parts of the following :

- (a) Draw the circuit of transistor in the CE configuration. Sketch the output characteristics. Indicate the active, saturation and cut off region. Explain each region in detail.



- (b) How BJT works as a switch ? Consider the transistor circuit of **Fig. 2** which has a resistance included between emitter and ground. Show that the transistor is operating in active mode. Calculate  $I_C$ ,  $I_E$  and  $I_B$ . Given :  $\beta = 50$ .

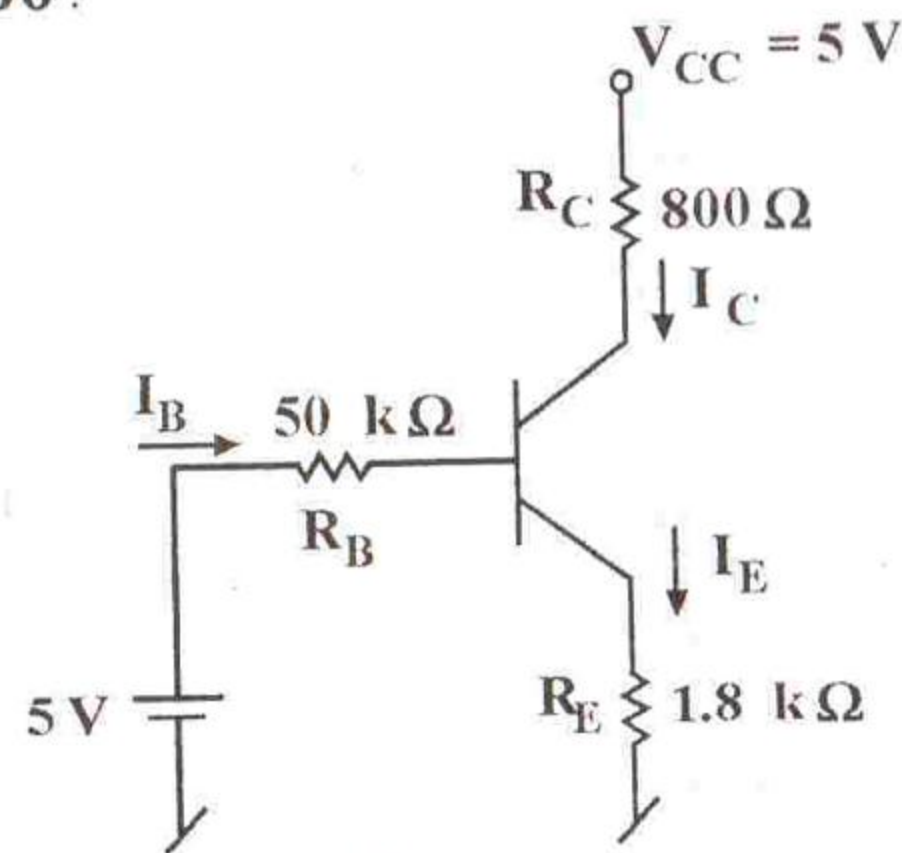


Fig. 2

- (c) Using the approximate h-parameter model, obtain the expression for a CE circuit for

- (1)  $A_i$
- (2)  $R_i$
- (3)  $A_v$
- (4)  $R_o$ .

4 Attempt any two parts of the following :

- (a) How is an FET used as a voltage - variable resistance ? Define : (1) transconductance  $g_m$ ; (2) drain resistance  $r_d$ ; (3) amplification factor  $\mu$  of an FET.

- (b) An n-channel JFET, having  $V_p = -4V$  and  $I_{DSS} = 10 \text{ mA}$ , is used in the circuit of Fig. 3. The parameter values are  $V_{DD} = 18 V$ ,  $R_S = 2 \text{ k}\Omega$ ,  $R_D = 2 \text{ k}\Omega$ ,  $R_1 = 450 \text{ k}\Omega$  and  $R_2 = 90 \text{ k}\Omega$ . Determine  $I_D$  and  $V_{DS}$ .

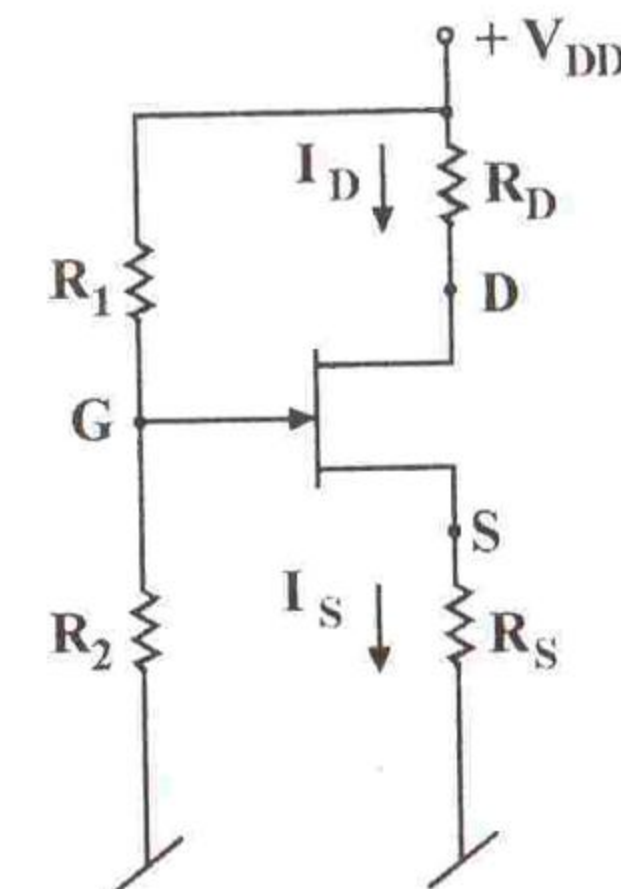


Fig. 3

- (c) Consider the n-channel enhancement MOSFET shown in Fig. 4. If  $V_T = 4V$  and  $I_D = 1.28 \text{ mA}$  at  $V_{GS} = 12V$ , determine the value of  $R_D$  for operation at  $V_{DS} = 8 V$ .



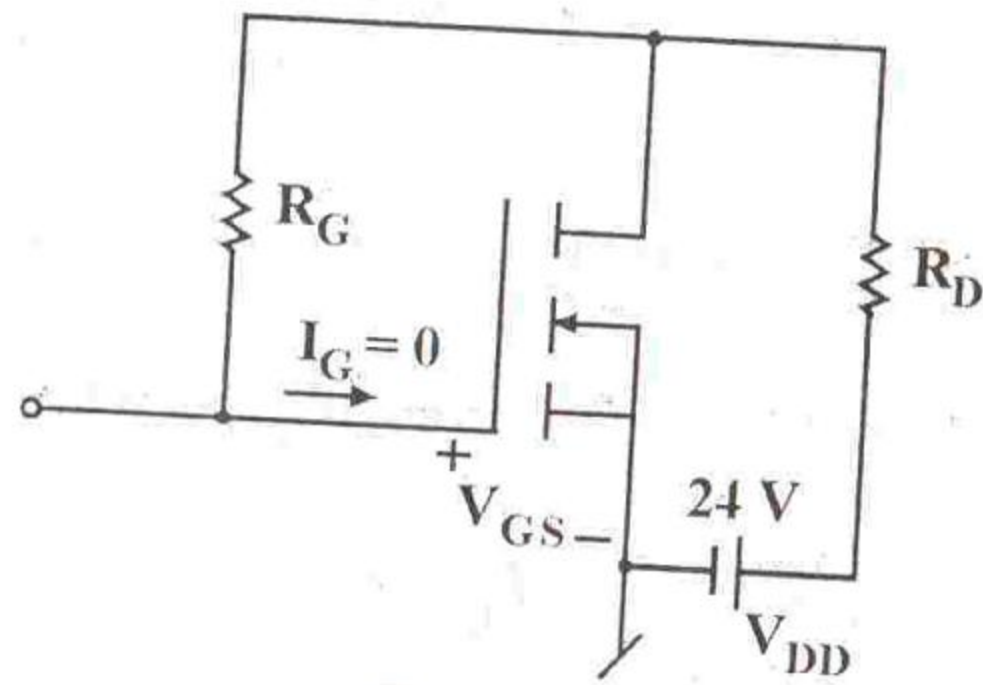


Fig. 4

Explain concept of pinch off.

- 5 Attempt any two parts of the following :
- (a) List characteristics of the ideal opamp. For the opamp circuit shown in Fig. 5. Find the values of  $R_1$  and  $R_2$  for the output to be

$$v_0 = -5 v_a + 3 v_b$$

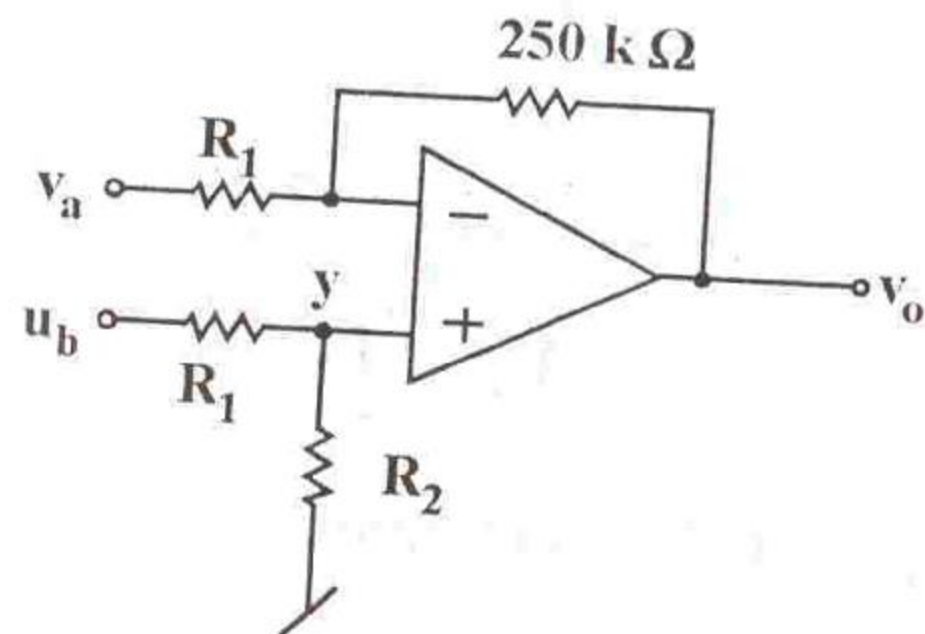


Fig. 5

(b) Write short notes :

- (1) Investing and noninvesting OPAMP
- (2) CMRR
- (3) Minterms and maxterms
- (4) BCD code and excess-3 code.

(c) (1) Given the boolean function

$$Y = (A + \bar{B}C)(C + AB)$$

Design a circuit using AND and OR gates to realize the above function.

(2) Convert the following :

$$(1010.101)_{10} \rightarrow ( )_2 \rightarrow ( )_4$$

$$(C3A.47)_H \rightarrow ( )_8 \rightarrow ( )_2$$

(3) Minimise the following using K-map :

$$f(a, b, c, d) = \sum m(0, 1, 3, 4, 7, 9, 10, 14, 15)$$

04

